
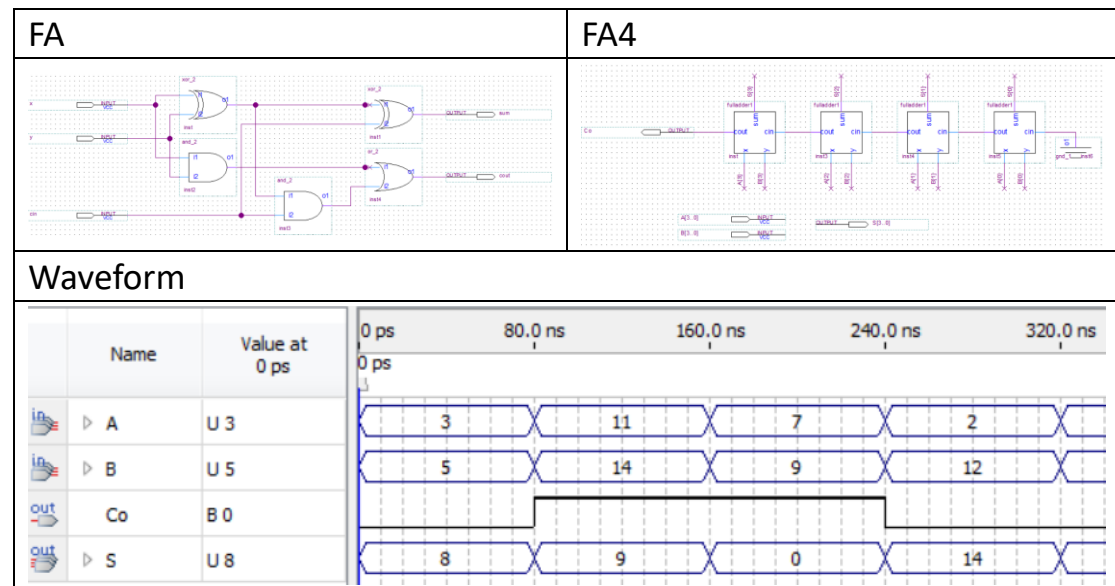



1. 4-bit adder

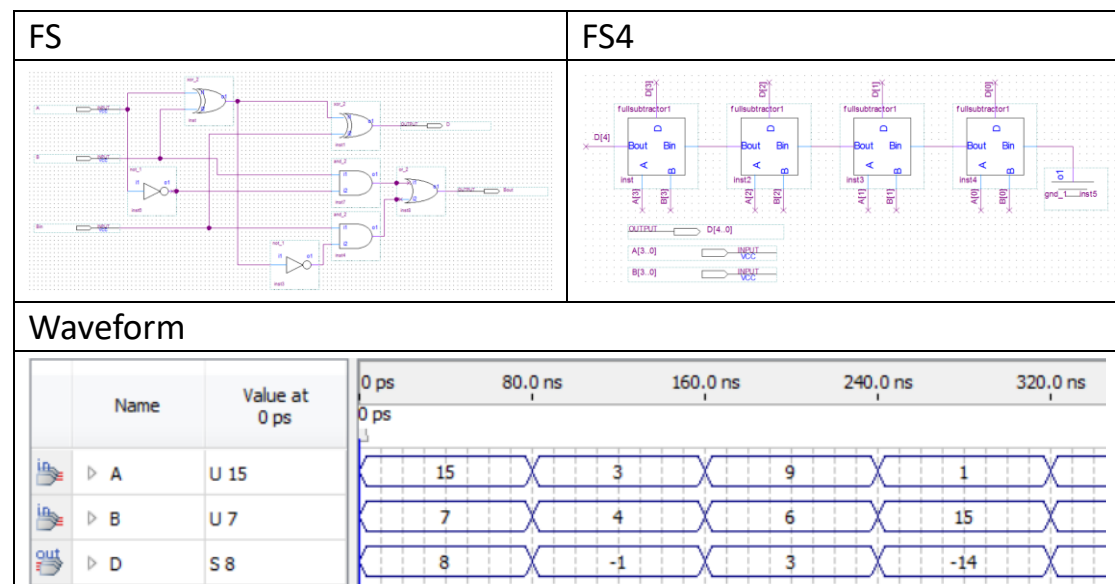



2. 4-bit subtractor



3. 4-bit multiplier

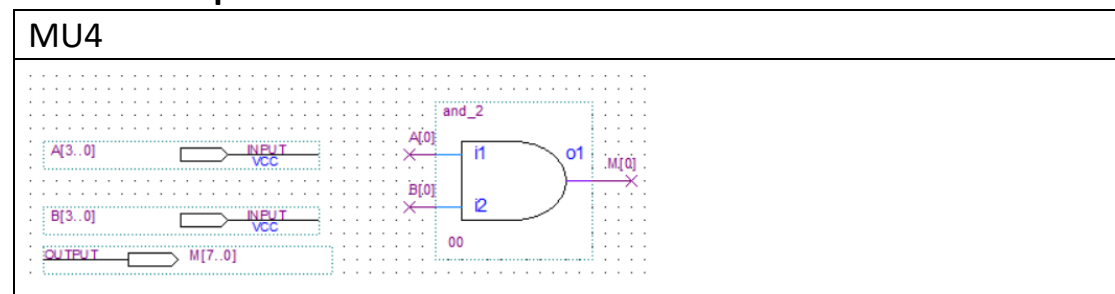

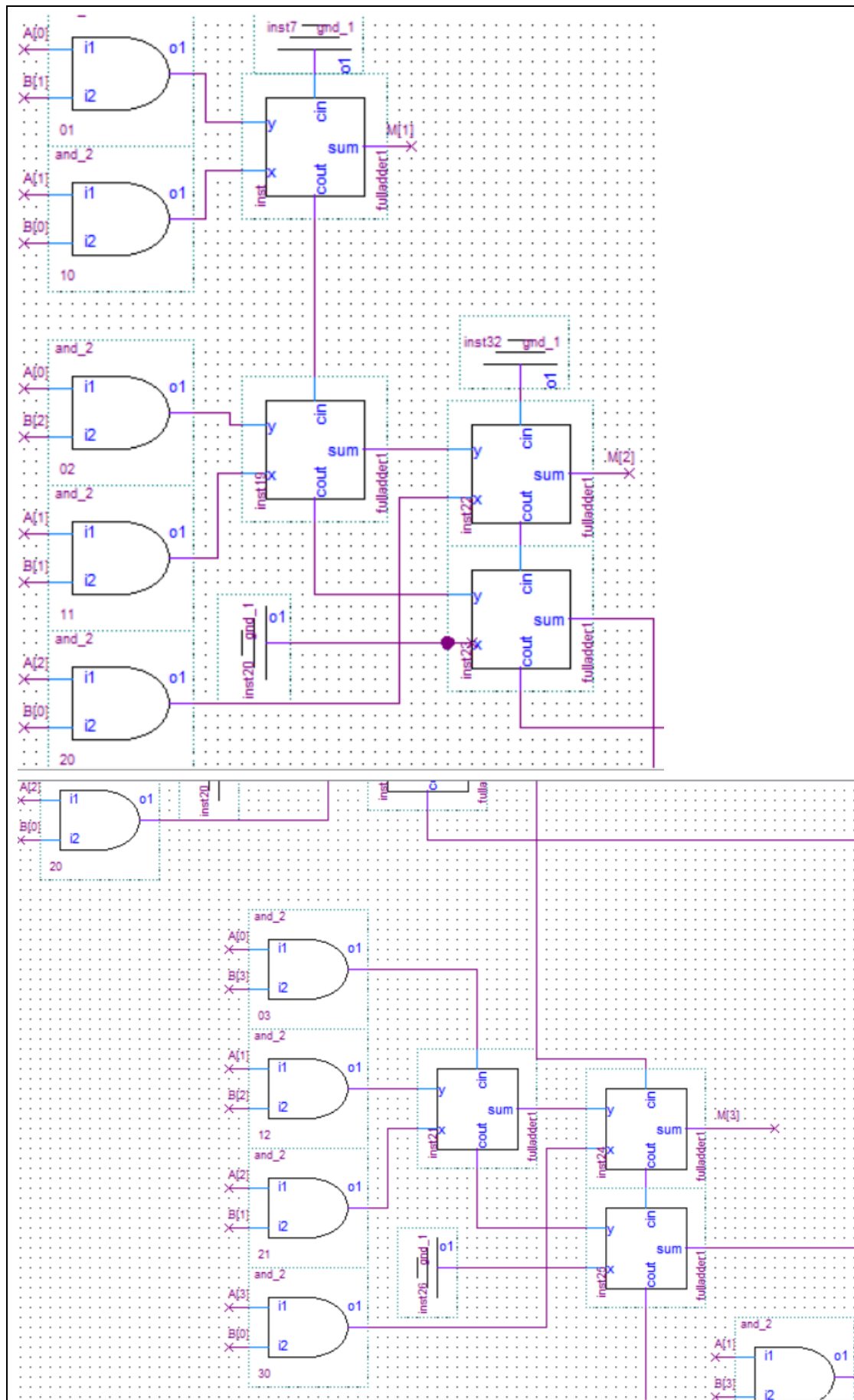

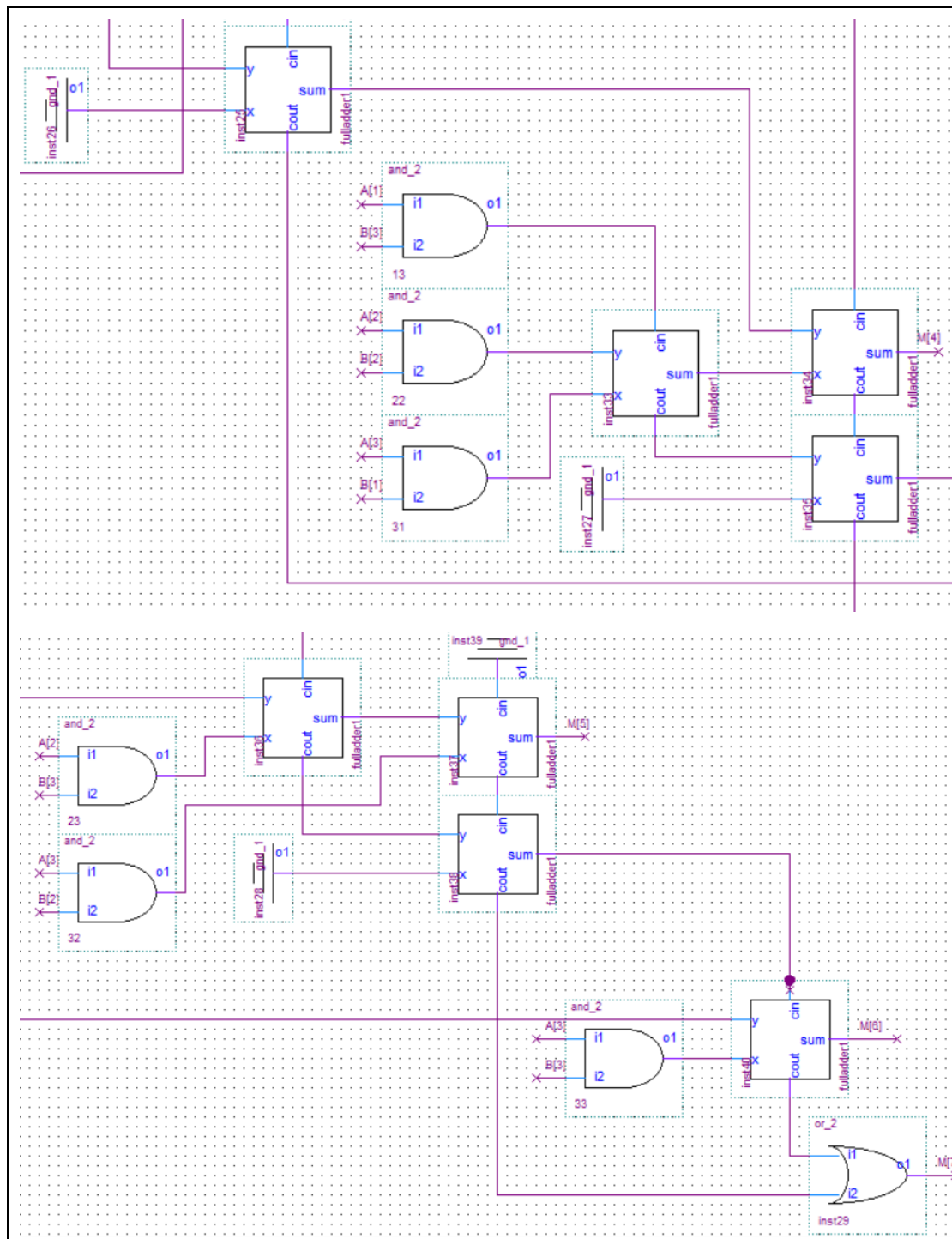

Waveform

